

Homework 4.

1. Draw logic circuit diagram
that circuit specified by No. 1.
Verilog description.

Module Circuit A (A, B, C, D, E)

Input A, B, C, D

Output E

Wire w, X, Y, Z, a, b;

1 OR X, B, C, D;

5 AND Y, a, b;

3 AND (w, z, b);

4 NOT z, Y, D;



2 NOT f, v, u;

not(a, b);

not(c, d);

combinative

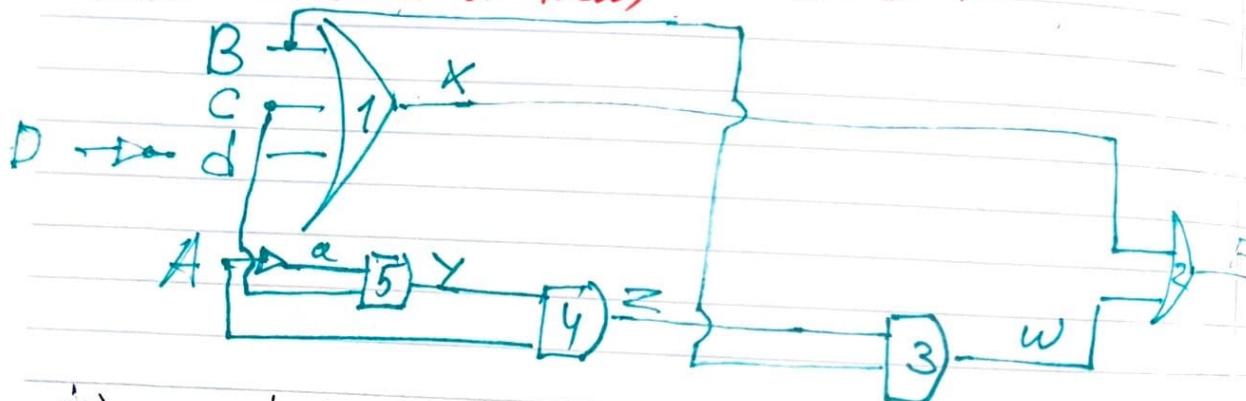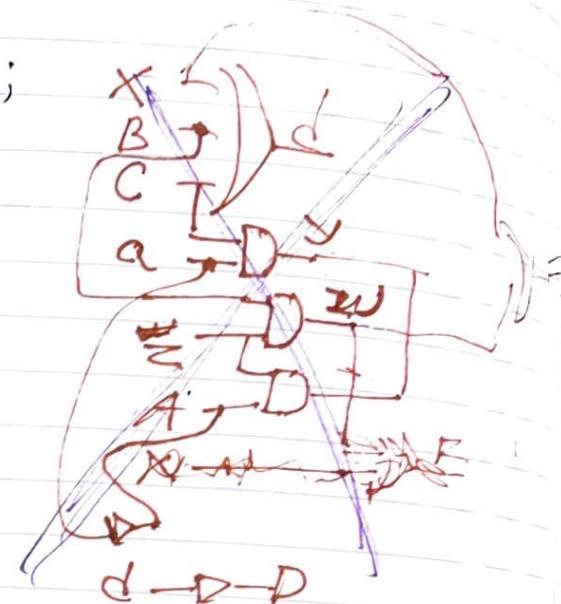! Here first is output letter in all of terms



b) module circuit B (y₁, y₂, y₃, a, b)

Output y₁, y₂, y₃;

Input a, b;

assign y₁ = a || b;


and (y₂, a, b);

assign y₃ = a & b;


end module

Here we assign right hand side expression to y₃.

It's data flow.

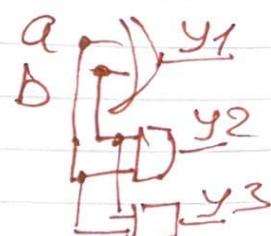

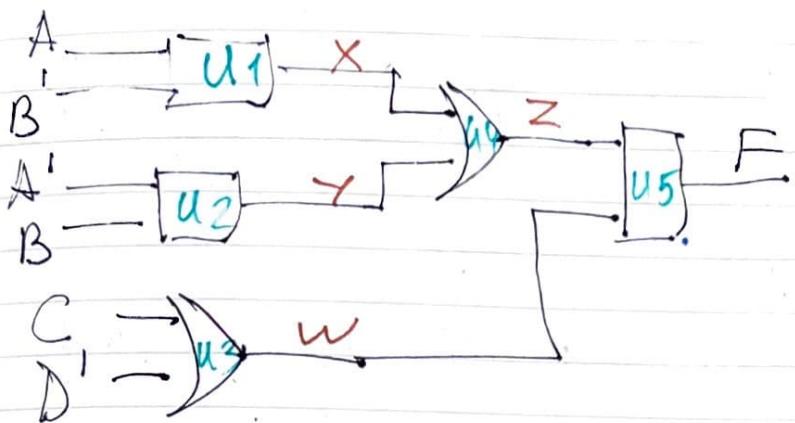2. a) Write a Verilog description of the circuit shown below.



```
module something(F, A, B', A', B, C, D');
    input A, A', B, B', C, D';
    output F;
    wire X, Y, Z, W;
    and U1(X, A, B');
    and U2(Y, A', B);
    or U3(W, C, D');
    or U4(Z, X, Y);
    and U5(F, Z, W);
endmodule
```

b) write a Verilog description of the circuit specified by the following Boolean function: $Z = (A + B') C' (C + D)$

```
module h(Z, A, B', C', C, D);
    input A, B', C', C, D;
    output Z;
    assign Z = (A | B') & C' & (C | D);
endmodule
```

Do Now


3: The adder-subtractor has the following

c) $M=0$ A $1100 = 12$
 B $1000 = 8$
 $\underline{1000} = 20$

d) $M=1$ A $0111 = 7$
 B $0110 = 6$
 $\underline{101} = 13$

c) $M=1$ A 0000
 B 0001
 $\underline{1110}$


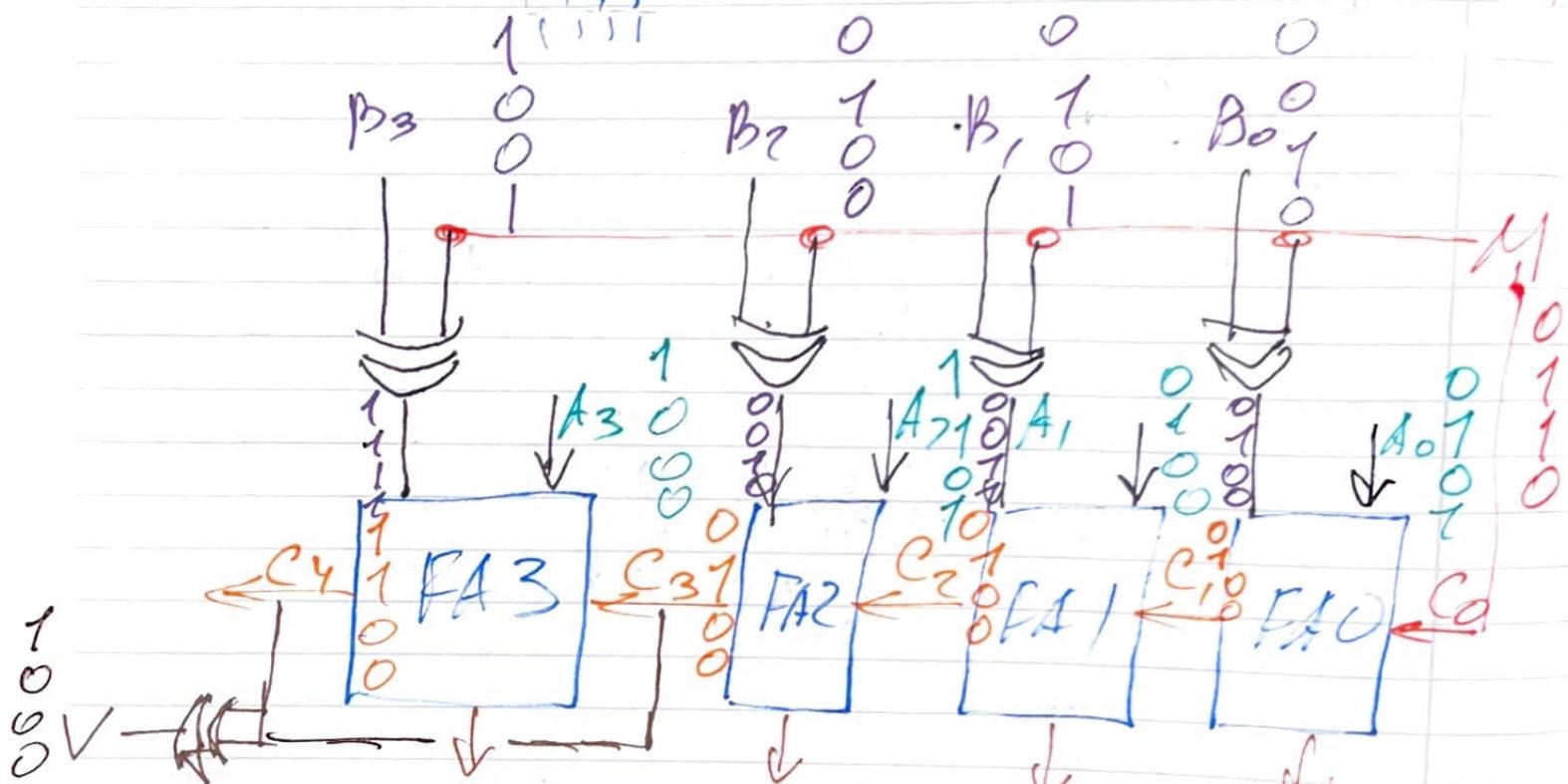
d) $M=0$ 0101
 1010
 $\underline{1111} \quad \boxed{0001} = -1$




	S_4	S_3	S_2	S_1	S_0
a)	1	0	1	0	0
b)	0	0	0	0	1
c)	1	1	1	1	1
d)	1	1	1	1	1

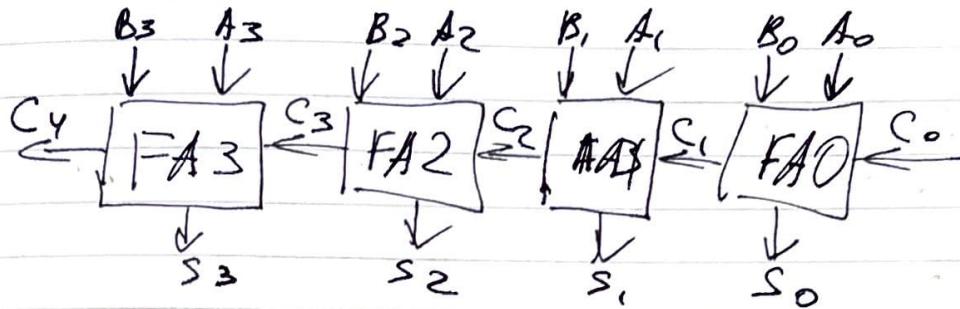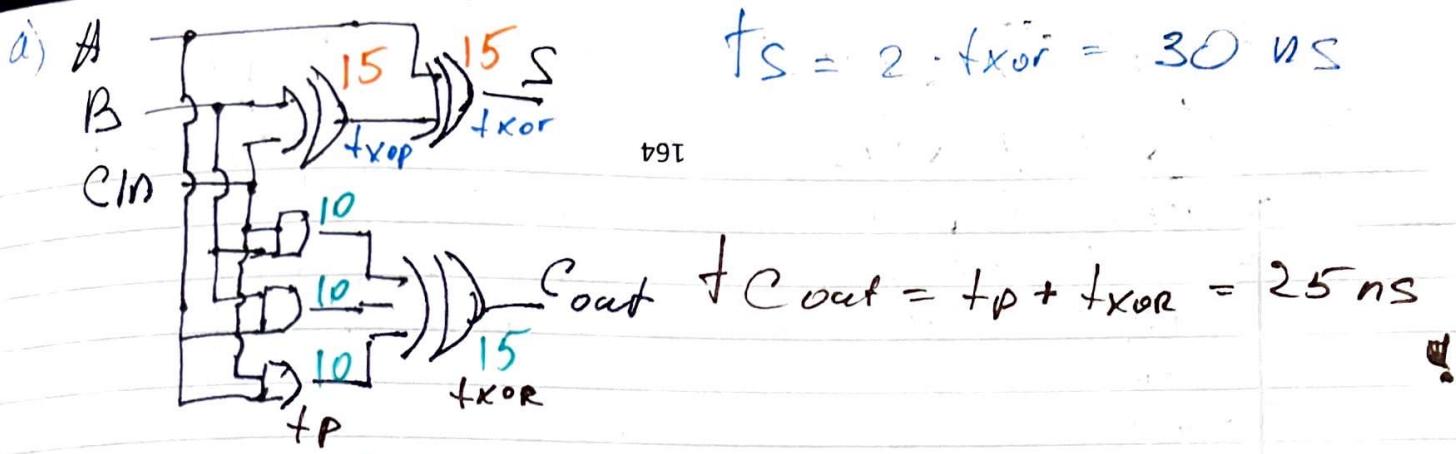4) Propogation delay: XOR = 15 ns

- AND and OR = 10 ns.
- What is propagation delay time of following 1-bit full adder,
 - 4-bit ripple carry adder build using 1-bit full adder;
 - 4 bit carry lookahead adder



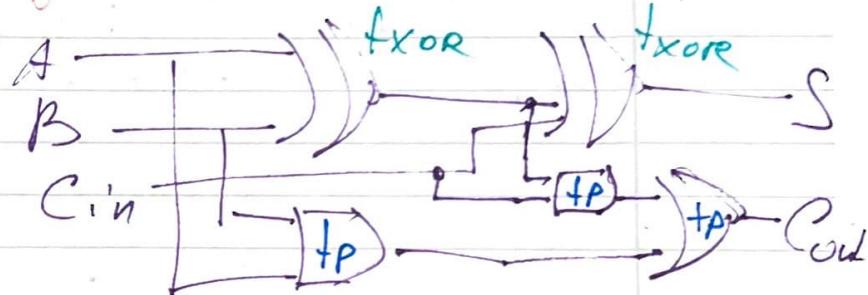Total Propagation Delay for Sum output = $(n-i)t_c + t_s$
 Total Propagation Delay for Carry Output = $n t_c$.



$$t_s = 4 \cdot 30 = 120 \text{ ns}$$


$$t_c = 3 \cdot 35 + 35 = 140 \text{ ns}$$

$$S_2 = (t_{\text{xor}} + 2t_p) + t_{\text{xor}}, \quad C_2 = (t_{\text{xor}} + 2t_p) + 2t_p$$

$$\text{Stable Carry output } C_4 = t_{\text{xor}} + 2 \cdot 4 \cdot t_p = 15 + 80 = 95$$

$$\text{Stable Sum output } S_4 = 2t_{\text{xor}} + 2(n-i) \cdot t_p = 30 + 60 = 90$$

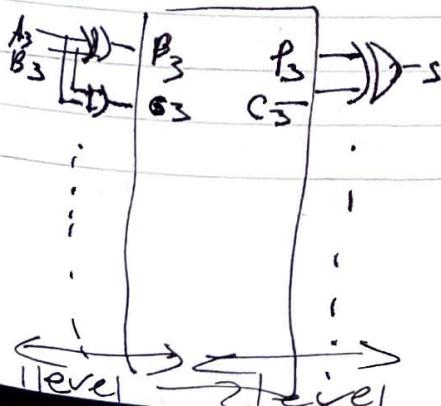c) Propagation Delay of Look Ahead Adder is faster than Ripple Adder because it is only 2 level gates.



Based on RGA logic circuit we gettings S out Cout and multiplying by 2.

$$t_s = 2 \cdot S = 2 \cdot 30 = 60 \text{ ns}$$

$$t_c = 2 \cdot \text{Cout} = 2 \cdot 35 = 70 \text{ ns}$$

$$5) F = \bar{A}' \cdot \bar{A} \cdot \bar{D} - (\bar{A} + BC)$$

$$F = \bar{A}' \cdot (\bar{A} + D') \cdot (\bar{A} + BC)$$

$$F = \bar{A} \cdot \bar{A} + \bar{A} \cdot \bar{D} \cdot (\bar{A} + BC)$$

$$F = \bar{A} \bar{A} \bar{D} + \bar{A} \bar{D} BC$$

$$F = \bar{A} \bar{D} + \bar{A} B C \bar{D}$$

$$F = \bar{A} \bar{D} (1 + BC)$$

$$F = \bar{A} \bar{D}$$

AB	00	01	11	10
00	1			
01	1			
11			1	
10				1

$\bar{A} \bar{D}$

$$G = (\bar{A} + BC)(\bar{A} \bar{D})$$

$$G = \bar{A} \bar{A} \bar{D} + \bar{A} \bar{D} BC$$


$$G = \bar{A}(A + \bar{D}) + (A + \bar{D})BC$$

$$G = 0 + \bar{A} \bar{D} + ABC + BC \bar{D}$$

$$G = \bar{A} \bar{D} + ABC$$


1	1	1
1	1	1
1	1	1
1	1	1

6)

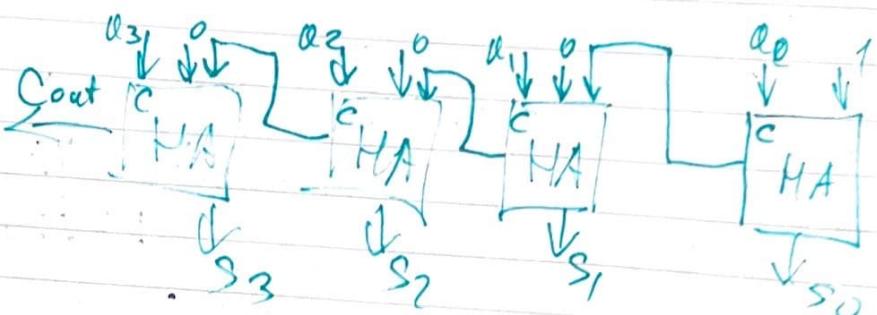

7)

A	B	XOR	XNOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

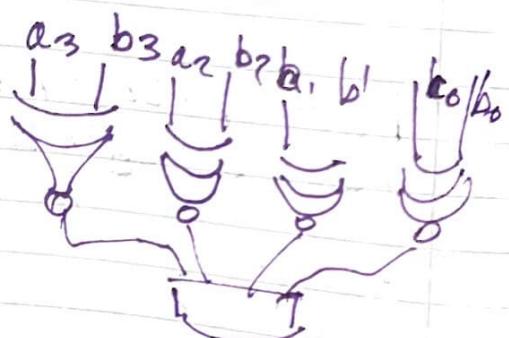


$$E = (a_3 \oplus b_3)' (a_2 \oplus b_2)' (a_1 \oplus b_1)' + (a_0 \oplus b_0)',$$

8) half subtractor

X	Y	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0
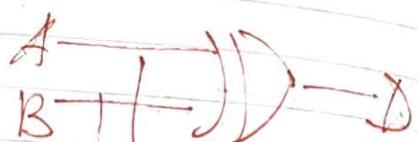
$$\begin{aligned} D &= X'Y + XY' \\ &= X \oplus Y \end{aligned}$$



$$B = X'Y$$

0	1
0	0


b) Full Subtractor

	B_{in}	D	B_{out}	x	y	Bin
0	0	0	0	0	0	00
0	0	1	1	1	0	01
0	1	0	1	0	1	10
0	1	1	0	1	1	11
1	0	0	1	0	0	10
1	0	1	0	0	0	11
1	1	0	0	0	0	00
1	1	1	1	1	1	01

$$D = x'y'B_{in} + x'yB_{in} + x'y'B_{in}' + x'yB_{in}' = x \oplus y \oplus B_{in}$$

0	1	1	1	1
0	0	1	1	0
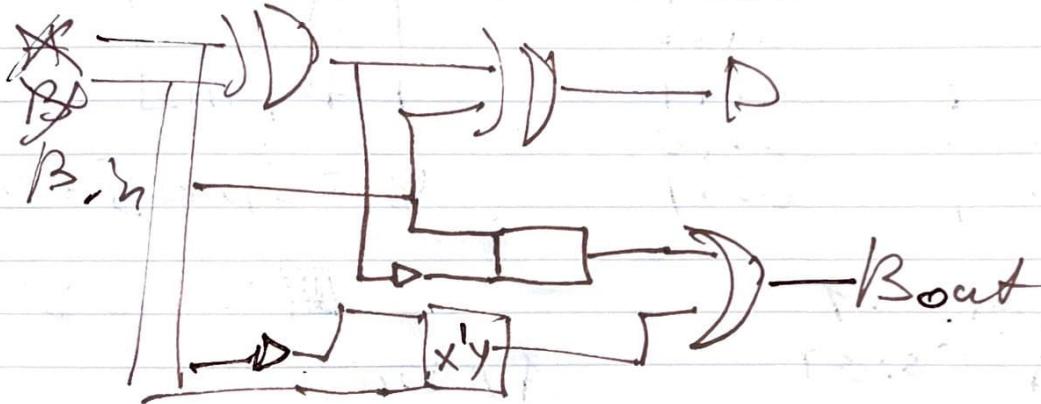
$$B_{out} = x'B_{in} \rightarrow x'y + yB_{in} = x'y + B_{in}(x \oplus y)$$



X	Y	Z	A	B	C	D	B_{out}	C_{out}
0	0	0	0	1	0	00	11	1
0	0	1	0	1	1	01	11	1
0	1	0	1	0	0	11	11	1
0	1	1	1	0	1	10	11	1
1	0	0	0	0	1	A = x'y +	B = x'y' +	C = xz + x'y'z
1	0	1	0	1	0	+yz	+y'z + xyz	= x ⊕ z
1	1	0	0	1	1			
1	1	1	1	0	0			

$$X = D - A$$

$$Y = D - Z$$

$$Z = D - C$$

$$X = D - C$$

$$X = D - A$$

$$Y = D - Z$$

$$Z = D - C$$

$$X = D - A$$

$$Y = D - Z$$

$$Z = D - C$$

Input


Output

A	B	C	D	w x y z
0	0	0	0	0 0 0 0
0	0	0	1	1 1 1 1
0	0	1	0	1 1 1 0
0	0	1	1	1 1 0 1
0	1	0	0	1 1 0 0
0	1	0	1	1 0 1 1
0	1	1	0	1 0 1 0
0	1	1	1	1 0 0 1
1	0	0	0	1 0 0 0
1	0	0	1	0 1 1 1
1	0	1	0	0 1 1 0
1	0	1	1	0 1 0 1
1	1	0	0	0 1 0 0
1	1	0	1	0 0 1 1
1	1	1	0	0 0 1 0
1	1	1	1	0 0 0 1




w
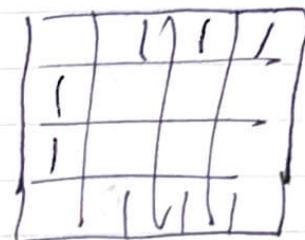
$$w = \bar{A}D + \bar{A}'C + A'B + AB'C'D$$



x

$$x = \bar{B}D + \bar{B}C + B\bar{C}D$$

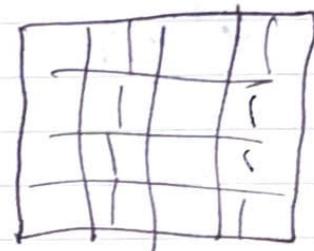

y

$$y = \bar{C}D + C\bar{D} = C \oplus D$$

Input +1

Z = D

A [3:0]

A [3:0]

